

# Solution: TP2


## Part I: Switches and Lights

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

```
ENTITY SwLeD IS
PORT(SW : IN STD_LOGIC_VECTOR(17 DOWNTO 0);
LEDR: OUT STD_LOGIC_VECTOR(17 DOWNTO 0));
END SwLeD;
```

```
ARCHITECTURE LALA OF SwleD IS
BEGIN
LEDR <= SW;
END LALA;
```


## Part II: Multiplexers

 


a) Circuit

s	m
0	x
1	y


b) Truth table

 

c) Symbol

 

a) Circuit

 

b) Symbol

```

library ieee;
use ieee.std_logic_1164.all;
entity Mux2to1 is
port( x: in std_logic_vector(7 downto 0);
      y: in std_logic_vector(7 downto 0);
      s: in std_logic;
      LEDR: OUT std_logic_vector(15 downto 0);
      m : out std_logic_vector(7 downto 0));
end Mux2to1;
architecture behaviore of Mux2to1 is


begin

m(0) <= ((not(s) and x(0)) or (y(0) and s));
m(1) <= ((not(s) and x(1)) or (y(1) and s));
m(2) <= ((not(s) and x(2)) or (y(2) and s));
m(3) <= ((not(s) and x(3)) or (y(3) and s));
m(4) <= ((not(s) and x(4)) or (y(4) and s));
m(5) <= ((not(s) and x(5)) or (y(5) and s));
m(6) <= ((not(s) and x(6)) or (y(6) and s));
m(7) <= ((not(s) and x(7)) or (y(7) and s));
LEDR<=y&x;

--LEDR(0)<=x(0);
--LEDR(1)<=x(1);
--LEDR(2)<=x(2);
--LEDR(3)<=x(3);
--LEDR(4)<=x(4);
--LEDR(5)<=x(5);
--LEDR(6)<=x(6);
--LEDR(7)<=x(7);
--LEDR(8)<=y(0);
--LEDR(9)<=y(1);
--LEDR(10)<=y(2);
--LEDR(11)<=y(3);
--LEDR(12)<=y(4);
--LEDR(13)<=y(5);
--LEDR(14)<=y(6);
--LEDR(15)<=y(7);
end behaviore;

```


### **Part III: Multiplexers**

 


a) Circuit

$s_2$	$s_1$	$s_0$	$m$
0	0	0	$u$
0	0	1	$v$
0	1	0	$w$
0	1	1	$x$
1	0	0	$y$
1	0	1	$y$
1	1	0	$y$
1	1	1	$y$

b) Truth table

 

c) Symbol

 

```

library ieee;
use ieee.std_logic_1164.all;
entity Mux5to1 is
port( u: in std_logic_vector(2 downto 0);
      v: in std_logic_vector(2 downto 0);
      w: in std_logic_vector(2 downto 0);
      x: in std_logic_vector(2 downto 0);
      y: in std_logic_vector(2 downto 0);
      LEDR: OUT std_logic_vector(14 downto 0);
      s0: in std_logic;
      s1: in std_logic;
      s2: in std_logic;
      m : out std_logic_vector(2 downto 0));


```

```

end Mux5to1;
architecture behaviore of Mux5to1 is
begin
m<=u when (S2='0' and S1='0' and S0='0') else
    v when (S2='0' and S1='0' and S0='1') else
    w when (S2='0' and S1='1' and S0='0') else
    x when (S2='0' and S1='1' and S0='1') else
    y when (S2='1' and S1='0' and S0='0') else
    y;
    LEDR<=y&x&w&v&u;
end behaviore;

```

### **Part IV: 7-segment decoder**

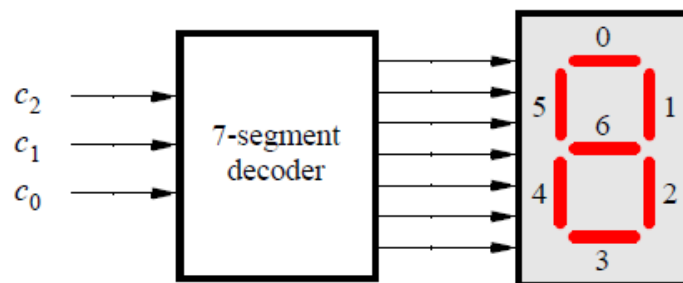

$c_2c_1c_0$	Character
000	H
001	E
010	L
011	O
100	
101	
110	
111	

Table 1. Character codes.

```

--7segemnts est a l'etat bas
LIBRARY ieee;
Use ieee.std_logic_1164.all;
entity segdisplay is
port ( VALUE : in bit_vector(2 downto 0);
DISPLAY : out bit_vector(6 downto 0));
end segdisplay;
architecture BEHAVIOUR of segdisplay is
begin
DISPLAY <= "0001001" when VALUE<="000" else
    "0000110" when VALUE<= "001" else


```

```

        "1000111" when VALUE<="010" else
        "1000000" when VALUE<="011" else
        "1111111" when VALUE<="100" else
        "1111111" when VALUE<="101" else
        "1111111" when VALUE<="110" else
        "1111111" when VALUE<="111" else
        "1111111";
end BEHAVIOUR;

```

### **Part V: 7-segment decoder**

 

```

LIBRARY ieee;
Use ieee.std_logic_1164.all;
entity decodseg is
port(sw0,sw1,sw2,sw3,sw4: in std_logic_vector(2 downto 0);
sw5,sw6,sw7: in std_logic;
sortie: out std_logic_vector(6 downto 0));
end decodseg;

```

```

architecture BEHAVIOUR of decodseg is
SIGNAL M : STD_LOGIC_VECTOR(2 DOWNTO 0);

```

```

COMPONENT Mux5to1 PORT (
    u: in std_logic_vector(2 downto 0);
    v: in std_logic_vector(2 downto 0);
    w: in std_logic_vector(2 downto 0);
    x: in std_logic_vector(2 downto 0);
    y: in std_logic_vector(2 downto 0);
    s0: in std_logic;
    s1: in std_logic;
    s2: in std_logic;
    m : out std_logic_vector(2 downto 0));
END COMPONENT;

```

```

COMPONENT segdisplay PORT ( VALUE1 : in std_logic_vector(2 downto 0);

```

```

DISPLAY : out std_logic_vector(6 downto 0));
END COMPONENT;

```

```

Begin

```

```

M0: Mux5to1 PORT MAP (sw0,sw1,sw2,sw3,sw4,sw5,sw6,sw7, M);

```

```

H0: segdisplay PORT MAP (M, sortie);

```

```

END BEHAVIOUR;

```

$SW_{17}$ $SW_{16}$ $SW_{15}$	Character pattern				
000	H	E	L	L	O
001	E	L	L	O	H
010	L	L	O	H	E
011	L	O	H	E	L
100	O	H	E	L	L

Table 2. Rotating the word HELLO on five displays.